



Indian Institute of Information Technology Vadodra

End-Sem Exam.: Basic Electronic Circuits (EC100) Time Duration: 60 Minutes & Max. Marks: 54 (+ 6 Bonus)

Note: You can make assumptions, however, you are requested to state your assumptions clearly and prove if required. Unless otherwise specified, assume Temp. = 300 K if required.

----- All The Best -----

Q. 1: A full wave bridge rectifier is designed using Si diodes. Each diode has a forward resistance of $120\ \Omega$. If input is a Sine wave with 24 V (peak-to-peak) and load resistance is of $1.76\ \text{K}\Omega$, then determine: (i) DC output voltage; (ii) RMS output voltage; and (iii) Actual rectification efficiency. Use diode model based on third approximation. (6)

Q. 2: In Fig. 1, find the resistance of Ge diode at this particular operating point. Consider the reverse saturation current of the diode is 100 nA. (3)

 


Fig. 1

 


Fig. 2

Q. 3: In voltage regulator circuit shown in Fig. 2, the Zener diode has $V_Z = 8\ \text{V}$, $I_{Z(\min)} = 500\ \mu\text{A}$, and $I_{Z(\max)} = 12\ \text{mA}$. Find the range of load resistor R so that the output voltage (V_{out}) remains constant 8 V without damaging the diode. (5)

Q. 4: In Fig. 3: (i) Draw the load line for first stage; and (ii) Find the Q-point of first stage. Further, using pi model, determine: (iii) Input resistance of first stage; (iv) Voltage gain of first stage; (v) AC voltage at node x. Consider the transistor is made of Silicon and Beta is 100. Hint: Z_{in} of second stage will act as R_L for first stage. (2+3+3+3+3)

 


Fig. 3

Q. 5: Find the exact voltage gain (V_{out}/V_{in}) of the circuit shown in Fig. 4. Consider the Op-amp is non-ideal and has an open loop gain of 200000. (2)

 


Fig. 4

 


Fig. 5

Q. 6: Find the output voltage (V_{out}) in Fig. 5, where $V_{out} = V_{o1} - V_{o2}$. Consider Op-amps are ideal. Hint: Use superposition theorem. (6)

Q. 7: The N-channel JFET shown in Fig. 6 has $V_P = 4$ V and $I_{DSS} = 10$ mA. Find the drain current (I_D) and drain voltage (V_D). (4)

 


Fig. 6

 


Fig. 7

Q. 8: Draw the load line of the circuit shown in Fig. 7. Also, find the Q-point (V_{DS} and I_D) of N-channel JFET and locate it on the load line. (4)

Q. 9: An nMOS has $V_{th} = 1$ V and $\mu_n \times C_{ox} \times (W/L) = 1$ mA/V². Determine the drain current (I_D) when: (i) $V_{GS} = 0.5$ V and $V_{DS} = 2$ V; (ii) $V_{GS} = 4$ V and $V_{DS} = 2$ V, and (iii) $V_{GS} = 4$ V and $V_{DS} = 4$ V. (1+2+2)

Q. 10: Implement the following Boolean expression using CMOS, where ' represents the NOT, . represents the AND and + represents the OR operations. (5)

$$Z = ((A + B) \cdot (C' + D \cdot E) + F) \cdot G$$

----- End -----